



# Digital Logic and System Design

## 5. Hardware Modelling and VHDL

COL215, I Semester 2024-2025

Venue: LHC 408

'E' Slot: Tue, Wed, Fri 10:00-11:00

Instructor: Preeti Ranjan Panda

[panda@cse.iitd.ac.in](mailto:panda@cse.iitd.ac.in)

[www.cse.iitd.ac.in/~panda/](http://www.cse.iitd.ac.in/~panda/)

Dept. of Computer Science & Engg., IIT Delhi

**VHDL**

**VHSIC** [Very High Speed Integrated Circuit]  
**Hardware Description Language**

# Contents

- Introduction
- Signal assignment
- Modelling delays
- Describing behaviour
- Structure, test benches, libraries, parameterisation
- Standards

# Hardware Description Languages


- VHDL - VHSIC (Very High Speed Integrated Circuit) Hardware Description Language
  - originally meant for simulation/documentation
  - syntax based on Ada/Pascal
- Verilog
  - syntax based on C
- SystemC
  - based on C++
  - system level language




# Which HDL to use?

- Coverage of Hardware concepts
  - equally good
- Learning one language eases learning of the other
  - most differences are minor/syntactic
- Status of tool support
  - equally good for both VHDL/Verilog
  - SystemC used more in system level modelling
 
# Fundamental VHDL Objects: entity/architecture pairs


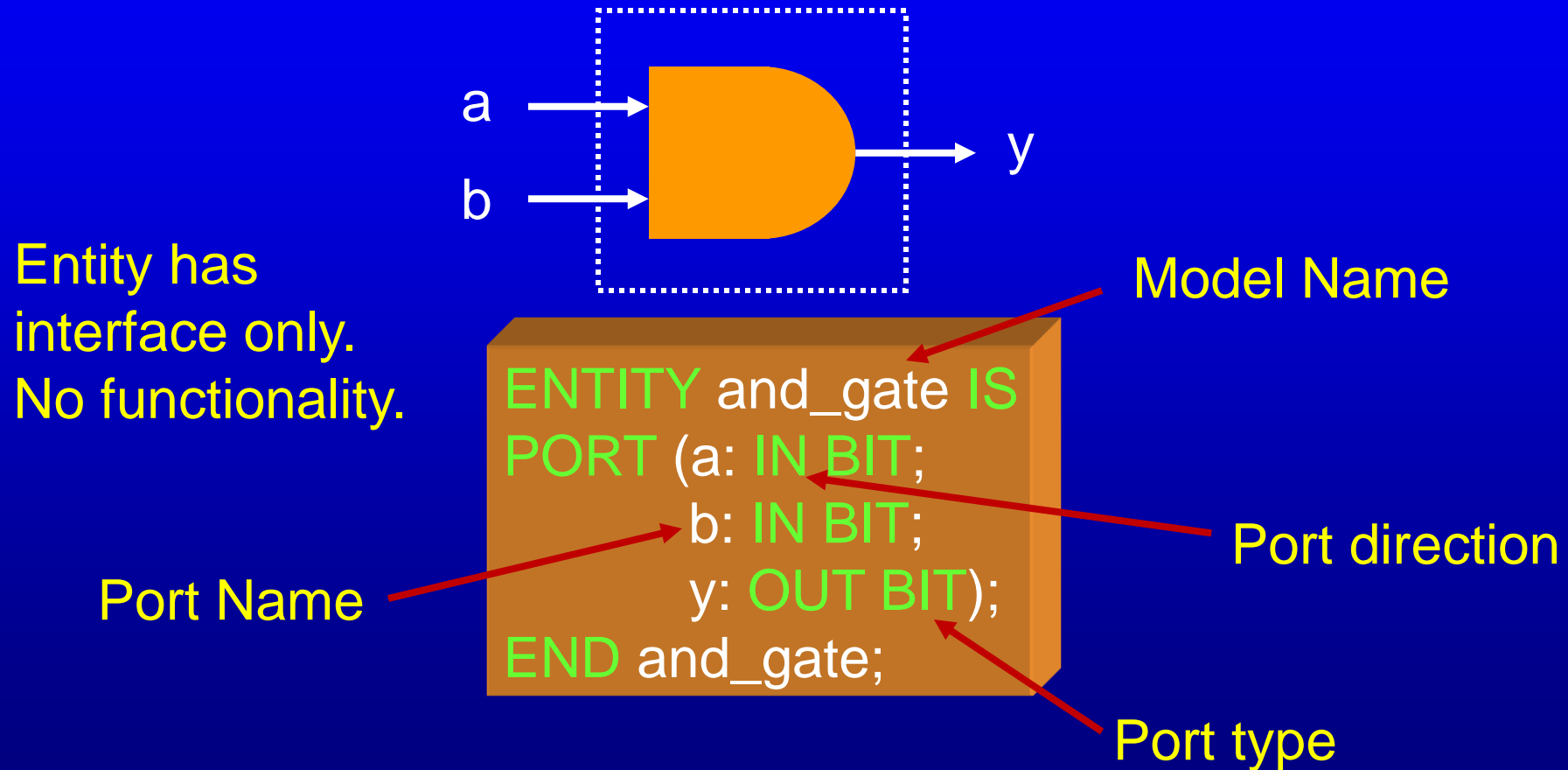
# Specifying interfaces: entities and ports



# Specifying Functionality: architectures

```
ARCHITECTURE data_flow OF and_gate IS  
BEGIN  
  y <= a AND b;  
END data_flow;
```

May have multiple architectures for given entity

- different views
- different levels of detail




# Contents

- Introduction
- Signal assignment
- Modelling delays
- Describing behaviour
- Structure, test benches, libraries, parameterisation
- Standards
 
# Specifying Concurrency: Concurrent Signal Assignment

```
ARCHITECTURE data_flow  
OF full_adder IS  
BEGIN  
    si <= ai XOR bi XOR ci;  
    co <= (ai AND bi) OR (bi AND ci)  
          OR (ai AND ci);  
END data_flow;
```



# When is Signal Assignment Executed?

Assignment executed when any signal on RHS changes

```
ARCHITECTURE data_flow  
OF full_adder IS  
BEGIN  
  si <= ai XOR bi XOR ci;  
  co <= (ai AND bi) OR (bi AND ci)  
        OR (ai AND ci);  
END data_flow;
```

Executed when  
ai, bi, or ci changes

Executed when  
ai, bi, or ci changes

# Order of Execution

- Execution independent of specification order


```
ARCHITECTURE data_flow  
OF full_adder IS  
BEGIN  
  si <= ai XOR bi XOR ci;  
  co <= (ai AND bi) OR (bi AND ci)  
        OR (ai AND ci);  
END data_flow;
```

```
ARCHITECTURE data_flow  
OF full_adder IS  
BEGIN  
  co <= (ai AND bi) OR (bi AND ci)  
        OR (ai AND ci);  
  si <= ai XOR bi XOR ci;  
END data_flow;
```

These two are equivalent
 
# Modelling Combinational Logic


- One concurrent assignment for each output




```
ARCHITECTURE data_flow  
OF comb_logic IS  
BEGIN  
  o1 <= i1 and i2;  
  o2 <= (i2 or i3) xor (i1 and i4);  
  o3 <= ...;  
  o4 <= ...;  
END data_flow;
```
 
# When Logic Complexity Increases

- Temporary SIGNALS needed
- Avoid redundant evaluations



Ports:  $x, y, z$

 

Signal:  $t$



# SIGNALS

- Represent intermediate wires/storage
- Internal - not visible outside entity

```
ENTITY comb_logic IS
PORT (i1, i2, i3, i4: IN BIT;
      o1, o2: OUT BIT);
END comb_logic;


ARCHITECTURE data_flow
OF comb_logic IS
BEGIN
  o1 <= (i1 and i2 and i3) xor i2;
  o2 <= (i1 and i2 and i3) or i4;
END data_flow;
```

```
ENTITY comb_logic IS
PORT (i1, i2, i3, i4: IN BIT;
      o1, o2: OUT BIT);
END comb_logic;

ARCHITECTURE data_flow1
OF comb_logic IS
  SIGNAL temp: BIT;
BEGIN
  temp <= (i1 and i2 and i3);
  o1 <= temp xor i2;
  o2 <= temp or i4;
END data_flow;
```
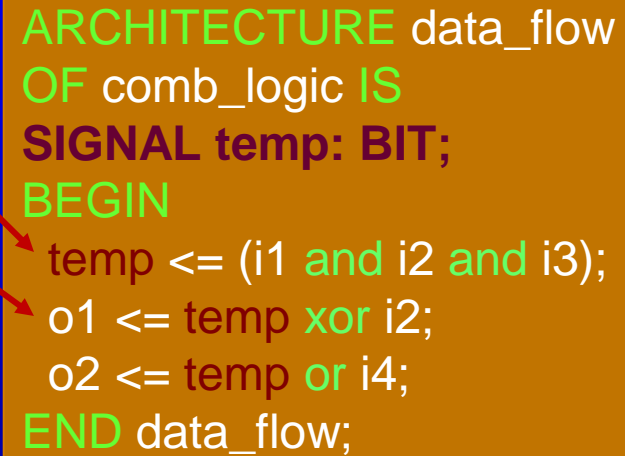
# SIGNALS

- executed when i1, i2, or i3 changes
- executed when temp or i2 changes
- SIGNALS are associated with time/waveforms
- PORT is a special type of SIGNAL



```
ARCHITECTURE data_flow  
OF comb_logic IS  
  SIGNAL temp: BIT;  
BEGIN  
  temp <= (i1 and i2 and i3);  
  o1 <= temp xor i2;  
  o2 <= temp or i4;  
END data_flow;
```


# Contents

- Introduction
- Signal assignment
- Modelling delays
- Describing behaviour
- Structure, test benches, libraries, parameterisation
- Standards
 
# Modelling Delays: inertial delay

- Models gate delays
- Spikes suppressed


```
y <= INERTIAL NOT a AFTER 10 ns;  
y <= NOT a AFTER 10 ns; -- inertial delay is default
```


 
# Modelling Delays: transport delay

- Models wires/transmission lines
  - used in more abstract modelling
- Spikes propagated

```
y <= TRANSPORT NOT a AFTER 10 ns;
```



# Events and Transactions

- Event
  - Signal assignment that causes change in value
- Transaction
  - Value scheduled for signal assignment
    - may or may not cause change in value




# Events and Transactions: Example

```
ARCHITECTURE demo OF example IS  
  SIGNAL a, b, c: BIT := '0';  
BEGIN  
  a <= '1' AFTER 15 NS;  
  b <= NOT a AFTER 5 NS;  
  c <= a AFTER 10 NS;  
END demo;
```


Source: Z. Navabi, VHDL - analysis and modeling of digital systems
 
# Events and Transactions: Example


```
ARCHITECTURE demo OF
example IS
SIGNAL a, b, c: BIT := '0';
BEGIN
  a <= '1' AFTER 15 NS;
  b <= NOT a AFTER 5 NS;
  c <= a AFTER 10 NS;
END demo;
```




Events  
and  
Transactions

 

Transactions  
Scheduled

 


Transaction  
Expires  
Event Created

 


Transaction  
Expires  
No Event
 
# Events and Transactions: Example

```
ARCHITECTURE demo OF  
example IS  
  SIGNAL a, b, c: BIT := '0';  
BEGIN  
  a <= '1' AFTER 15 NS;  
  b <= NOT a AFTER 5 NS;  
  c <= a AFTER 10 NS;  
END demo;
```




Events  
and  
Transactions

 

 
# Inertial Delay: Suppressing a pulse


```
SIGNAL a, b: BIT := '0';  
...  
a <= '1' AFTER 10 NS,  
    '0' AFTER 15 NS; -- transport  
b <= NOT a AFTER 8 NS; -- inertial
```



Events  
and  
Transactions

 


Transactions  
Scheduled

 


Transaction  
Expires  
Event Created
 
# Inertial Delay: Suppressing a pulse

```
SIGNAL a, b: BIT := '0';  
...  
a <= '1' AFTER 10 NS,  
    '0' AFTER 15 NS; -- transport  
b <= NOT a AFTER 8 NS; -- inertial
```




Events  
and  
Transactions

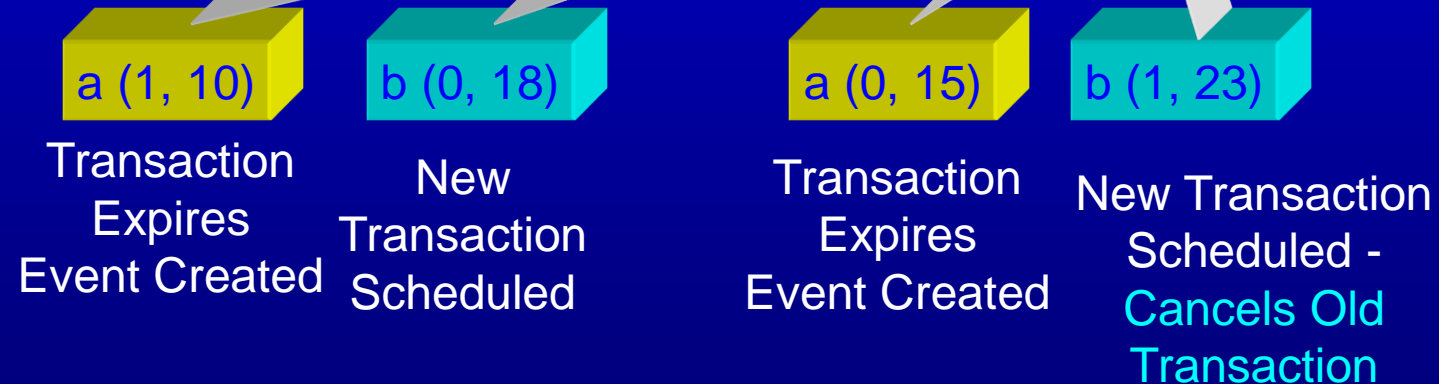
 
# Inertial Delay: Suppressing a pulse

```
SIGNAL a, b: BIT := '0';  
...  
a <= '1' AFTER 10 NS,  
    '0' AFTER 15 NS; -- transport  
b <= NOT a AFTER 8 NS; -- inertial
```



Events  
and  
Transactions


b (1,23)

Transaction  
Expires  
No Event



 
# Transport Delay: Propagating a pulse

```
SIGNAL a, b: BIT := '0';  
...  
a <= '1' AFTER 10 NS, '0' AFTER 15 NS; -- transport  
b <= TRANSPORT NOT a AFTER 8 NS;
```




Events  
and  
Transactions

 
 
# Transport Delay: Propagating a pulse

```
SIGNAL a, b: BIT := '0';  
...  
a <= '1' AFTER 10 NS, '0' AFTER 15 NS; -- transport  
b <= TRANSPORT NOT a AFTER 8 NS;
```




Events  
and  
Transactions



 
# Transport Delay: Propagating a pulse

```
SIGNAL a, b: BIT := '0';  
...  
a <= '1' AFTER 10 NS, '0' AFTER 15 NS; -- transport  
b <= TRANSPORT NOT a AFTER 8 NS;
```



Events  
and  
Transactions

 

Transaction  
Expires  
Event Created



Transaction  
Expires  
Event Created

# Generating Periodic Waveforms: Clocks



```
a <= NOT a AFTER 10 ns;
```

# Delta Delays

```
ARCHITECTURE x of y IS  
  SIGNAL b, c: bit;  
BEGIN  
  b <= NOT a;  
  c <= clock NAND b;  
  d <= c AND b;  
END x;
```

zero-delay  
signal assignments

a <= 0  
(clock = 1,  
b=0, c=1,d=0)

Delta 1

b <= 1

Delta 2

c <= 0  
d <= 1

Delta 3

d <= 0

Delta 4



Simulation time does not advance

# Contents

- Introduction
- Signal assignment
- Modelling delays
- Describing behaviour
- Structure, test benches, libraries, parameterisation
- Standards



# Describing Behaviour: Processes

- Signal assignment statements OK for simple behaviour
- Complex behaviour requires more constructs
  - conditionals (IF, CASE)
  - loops (FOR, WHILE)
- Use VHDL PROCESS

# VHDL PROCESS

- Execution within a PROCESS is sequential
- Processes are concurrent w.r.t each other
- Signal assignment is a simple special case
- Architecture consists of a set of Processes (and signal assignments) at top level
- Processes communicate using signals

ARCHITECTURE x of a IS BEGIN

f <= g+ 1;

p1: PROCESS  
BEGIN  
IF (x) THEN ...  
ELSE ...;  
END PROCESS;

p2: PROCESS  
BEGIN  
FOR i in 1 TO 5 LOOP  
a (i) <= 0;  
END LOOP;...  
END PROCESS;

END x;


# PROCESS Execution Semantics

- Need to define when Process is executed
  - suspending/resuming execution
  - more complex than signal assignment (“evaluate when any signal on RHS changes”)
- No notion of “completion” of execution
  - needs to emulate hardware

# Process Sensitivity List


- Process is sensitive to signals on Sensitivity List
- All processes executed once at time=0
- Suspended at end of process
- Reactivated when event occurs on any signal in sensitivity list

Sensitivity List

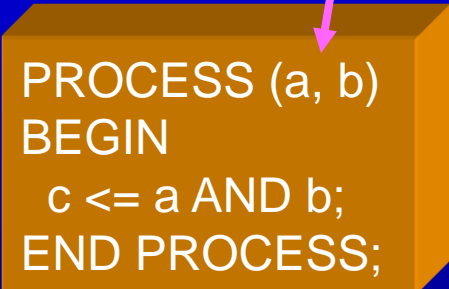

```
PROCESS (a, b)
BEGIN
  c <= a AND b;
END PROCESS;
```


# Process and Signal Assignment

 

Need not use PROCESS for modelling simple combinational behaviour
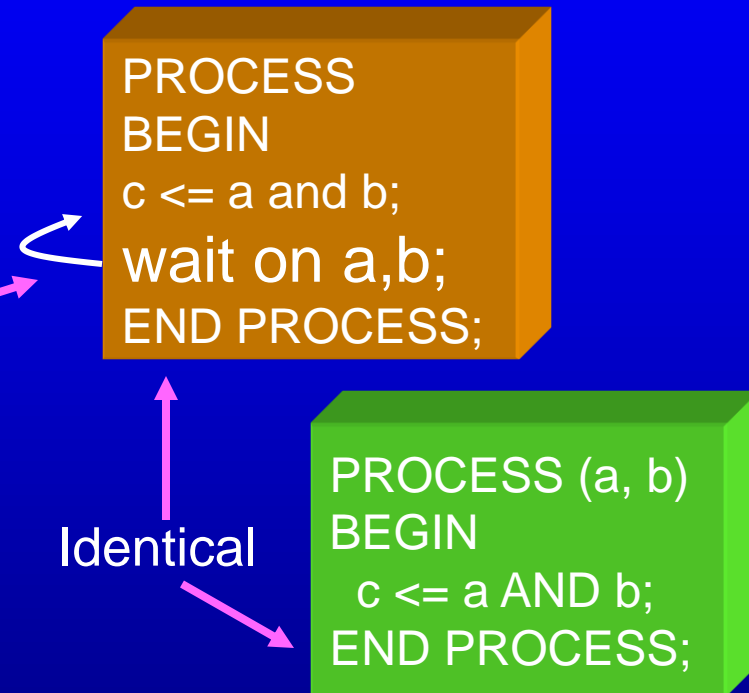
# Process Synchronisation

- Sensitivity list is optional
- **wait** is general synchronisation mechanism
- Implicit infinite loop in process
- Execution continues until suspended by **wait** statement



# Synchronisation with WAITs

- Synchronisation with wait more flexible
- Both sensitivity list and wait not allowed in same process
  - process can have any number of waits
- For combinational logic, place ALL input signals in sensitivity list
- For sequential logic, use waits appropriately

# WAIT Examples

```
PROCESS  
BEGIN  
  wait for 10 ns;  
  outp <= inp;  
END PROCESS
```

Sample input every 10 ns

```
PROCESS  
BEGIN  
  wait until clk'event and clk='1';  
  q <= d;  
END PROCESS
```

Edge triggered flip flop

```
PROCESS (clk, reset)  
BEGIN  
  IF reset THEN  
    q <= '0';  
  ELSIF clk'event and clk='1'  
    q <= d;  
  END IF;  
END PROCESS
```

Flip flop with Reset

```
PROCESS  
BEGIN  
  outp <= inp;  
END PROCESS
```

Error! (no waits)  
(Compare signal  
assignment at  
architecture level)



# Process Variables

- Variables used for local computations
  - within processes
- Not associated with events/transactions
  - unlike signals
- Assignment of value is immediate
  - unlike signals

```
PROCESS
VARIABLE result : BIT;
BEGIN
wait until clk'event and clk='1';
result := '0';
for i in 0 to 6 loop
    result := result XOR inp (i);
end loop;
outp <= result;
END PROCESS;
```

# Signal Assignments in Processes

```
PROCESS (x)
BEGIN
  A <= '1';
  A <= '0'; -- overrides
END PROCESS;
```

Multiple  
assignments OK.  
Sequential  
Execution.

```
PROCESS
BEGIN
  -- A='0' here
  A <= '1';
  B <= A; -- B='0'
  wait on x;
END PROCESS;
```

Signal  
assignments  
take effect  
when process  
suspends  
(next delta)

```
PROCESS
VARIABLE p: BIT;
BEGIN
  -- A='0' here
  A <= '1';
  p := A; -- p='0'
  B <= p; -- B='0'
  wait on x;
END PROCESS;
```

Variable assignments  
take effect immediately  
(same delta)

# Signal Assignments in Processes

```
PROCESS  
VARIABLE p: BIT;  
BEGIN  
  A <= '0';  
  if (c) then A <= '1';  
  else begin  
    p := B;  
    A <= p;  
  end  
  wait on x;  
  B <= A;  
  A <= B;  
  wait on x;  
END PROCESS;
```

Signal Assignment  
to A equivalent to:

1. Introduce  
temporary  
variable tA  
when A occurs  
on LHS
2. Assign ta to A  
when process  
suspends

Equivalent

```
PROCESS  
VARIABLE p, tA, tB: BIT;  
BEGIN  
  tA := '0';  
  if (c) then tA := '1';  
  else begin  
    p := B;  
    tA := p;  
  end  
  A <= tA;  
  wait on x;  
  tB := A;  
  tA := B;  
  A <= tA;  
  B <= tB;  
  wait on x;  
END PROCESS;
```

# Contents


- Introduction
- Signal assignment
- Modelling delays
- Describing behaviour
- Structure, test benches, libraries, parameterisation
- Standards

# Structural Description



- Instantiation
- Interconnection
 
# Hierarchy

```
ENTITY x IS  
  PORT (a, b: IN BIT,  
        c: OUT BIT);  
END x;  
ARCHITECTURE xa OF x IS  
BEGIN  
  c <= a AND b;  
END xa;
```



  
```
ENTITY y IS  
  PORT (a : IN BIT,  
        b: OUT BIT);  
END y;  
ARCHITECTURE ya OF y IS  
BEGIN  
  b <= NOT a;  
END ya;
```



z contains  
instances of  
x and y
 
# Instantiation and Interconnection - 1

```
ENTITY z IS
  PORT (p, q: IN BIT,
        r: OUT BIT);
END z;
ARCHITECTURE structural OF z IS
  COMPONENT xc
    PORT (a, b: IN BIT; c: OUT BIT);
  END COMPONENT;
  COMPONENT yc
    PORT (a: IN BIT; c: OUT BIT);
  END COMPONENT;
  FOR ALL: xc USE WORK.x (xa);
  FOR ALL: yc USE WORK.y (ya);
  SIGNAL t: BIT;
BEGIN
  x1: xc PORT MAP (p, q, t);
  y1: yc PORT MAP (t, r);
END structural;
```



Component declaration

Configuration specification  
(which architecture?)

Temporary signal

Instantiation

# Instantiation and Interconnection - 2

Instance name


Component name

```
x1: xc PORT MAP (p, q, t);  
y1: yc PORT MAP (t, r);
```

Same name  
implies connection

Port association list:  
order of names  
determines connectivity:

a - p  
b - q  
c - t

 



# Port Mapping

```
COMPONENT xc  
  PORT (a, b: IN BIT; c: OUT BIT);  
END COMPONENT;
```

Mapping by position: preferred for short port lists

```
x1: xc PORT MAP (p, q, t);
```

Mapping by name: preferred for long port lists

```
x1: xc PORT MAP (b => q, a => p, c => t);
```


In both cases, complete port mapping should be specified

# Test Benches

- Purpose - test correctness of Design Under Test (DUT)
  - provide input stimulus
  - observe outputs
  - compare against expected outputs
- Test Bench is also a VHDL model

 
# Test Bench Modelling - 1

- Test bench a separate VHDL entity
- Ports are connected to DUT's ports
  - i/p port corresponding to DUT's o/p port
  - o/p port corresponding to DUT's i/p port


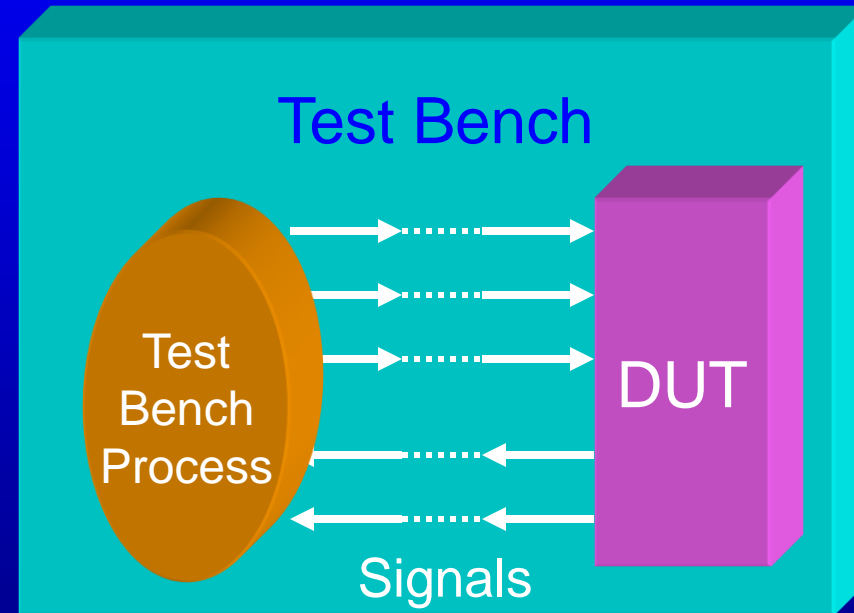
# Test Bench Modelling - 2

- Test bench instantiates the DUT
- Stimulus generation and output monitoring in separate VHDL process
- Signals are connected to DUT's ports



# Libraries and Packages

- **PACKAGE** - collection of
  - components
  - data types
  - functions/procedures
- **LIBRARY** - collection of **PACKAGES**

# Packages

```
PACKAGE util IS  
  COMPONENT c IS  
    PORT (a: IN BIT, b: OUT BIT);  
  END COMPONENT  
  TYPE my_int IS INTEGER RANGE -7 TO 7;  
  FUNCTION comp (a: BIT_VECTOR)  
    RETURN BIT_VECTOR;  
END util;
```

Package declaration

```
PACKAGE BODY util IS  
  FUNCTION comp (a: BIT_VECTOR)  
    RETURN BIT_VECTOR IS  
  BEGIN  
    RETURN NOT a;  
  END comp;  
END util;
```


Package body

# Using a Package

```
PACKAGE util IS
  COMPONENT c IS
    PORT (a: IN BIT, b: OUT BIT);
  END COMPONENT
  TYPE my_int IS INTEGER RANGE -7 TO 7;
  FUNCTION comp (a: BIT_VECTOR)
    RETURN BIT_VECTOR;
END util;
...
```

Library Name      Package Name      All Contents
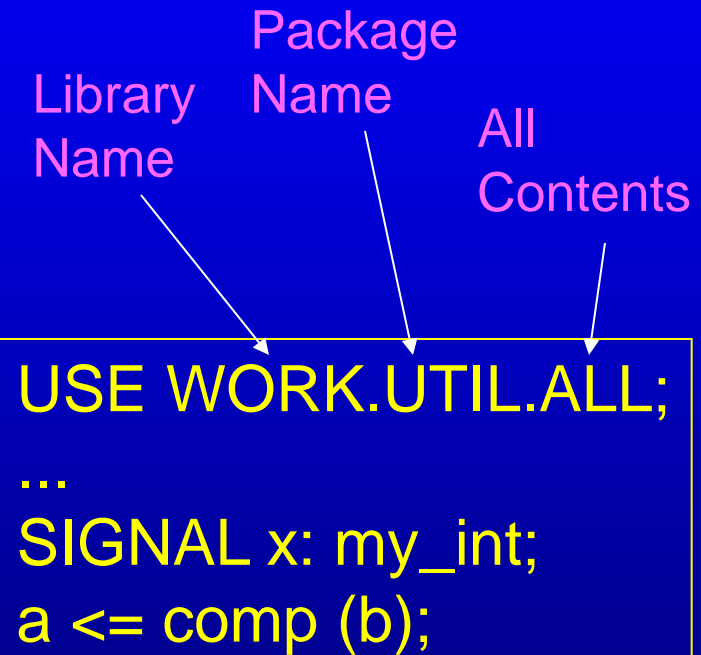
```
USE WORK.UTIL.ALL;
...
SIGNAL x: my_int;
a <= comp (b);
```



# Libraries

- **STD**
  - STANDARD
    - types/utilities (BIT, TIME, INTEGER,...)
  - TEXTIO
    - interface to text files
- **WORK**
  - default library for storing user designs
- **STD\_LOGIC\_1164**
  - multi-valued logic



# TEXTIO Package

- Data types and functions for
  - reading from text files
  - writing out text files

```
FILE f: TEXT IS "file_name";  
VARIABLE one_line: line;  
VARIABLE str: STRING;  
...  
READLINE (f, one_line); -- read one line from file  
READ (str, one_line); -- read a word from line  
WRITELINE (g, one_line); -- write one line to file  
WRITE (str, one_line); -- write a word into line
```

# Design Parameterisation: GENERICS

```
ENTITY e IS
  GENERIC (delay: TIME := 2 NS; width: INTEGER := 4);
  PORT (a: IN BIT_VECTOR (0 TO width);
        b: OUT BIT_VECTOR (0 TO width));
END e;

ARCHITECTURE a OF e IS
BEGIN
  b <= NOT a AFTER delay;
END a;
```

Default  
Value

Generic  
Parameters

# Passing GENERIC Parameters

```
ENTITY c IS  
  GENERIC (delay: TIME := 4 ns); PORT (a: IN BIT; b: OUT BIT);  
END c;
```

```
ARCHITECTURE a OF e IS  
  COMPONENT c  
    GENERIC (t: TIME:= 4 NS);  
    PORT (a: IN BIT, b: OUT BIT);  
  END COMPONENT;  
  SIGNAL x, y: BIT;  
  FOR ALL: c USE work.c (arc);  
  BEGIN  
    c1: c GENERIC MAP (3 ns)  
      PORT MAP (x, y);  
  END a;
```


```
ARCHITECTURE def OF e IS  
  COMPONENT c  
    GENERIC (t: TIME:= 4 NS);  
    PORT (a: IN BIT, b: OUT BIT);  
  END COMPONENT;  
  SIGNAL x, y: BIT;  
  FOR ALL: c USE work.c (arc);  
  BEGIN  
    c1: c PORT MAP (x, y);  
  END def;
```

Delay parameter = 3 ns

Default Delay = 4 ns
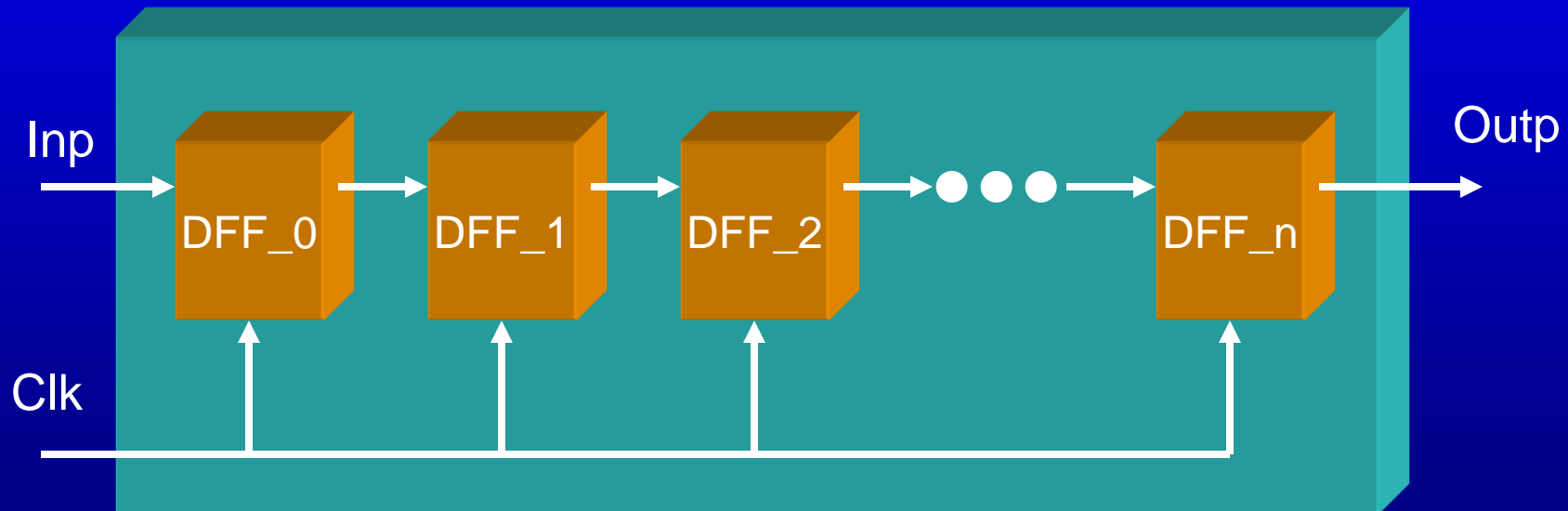
# Conditional and Looped Instantiation

Number of instances of DFF determined by Generic Parameter  $n$




# Conditional and Looped Instantiation: GENERATE

```
GENERIC (n: INTEGER)...
```

```
...
```


```
SIGNAL t: BIT_VECTOR (0 TO n-1);
```

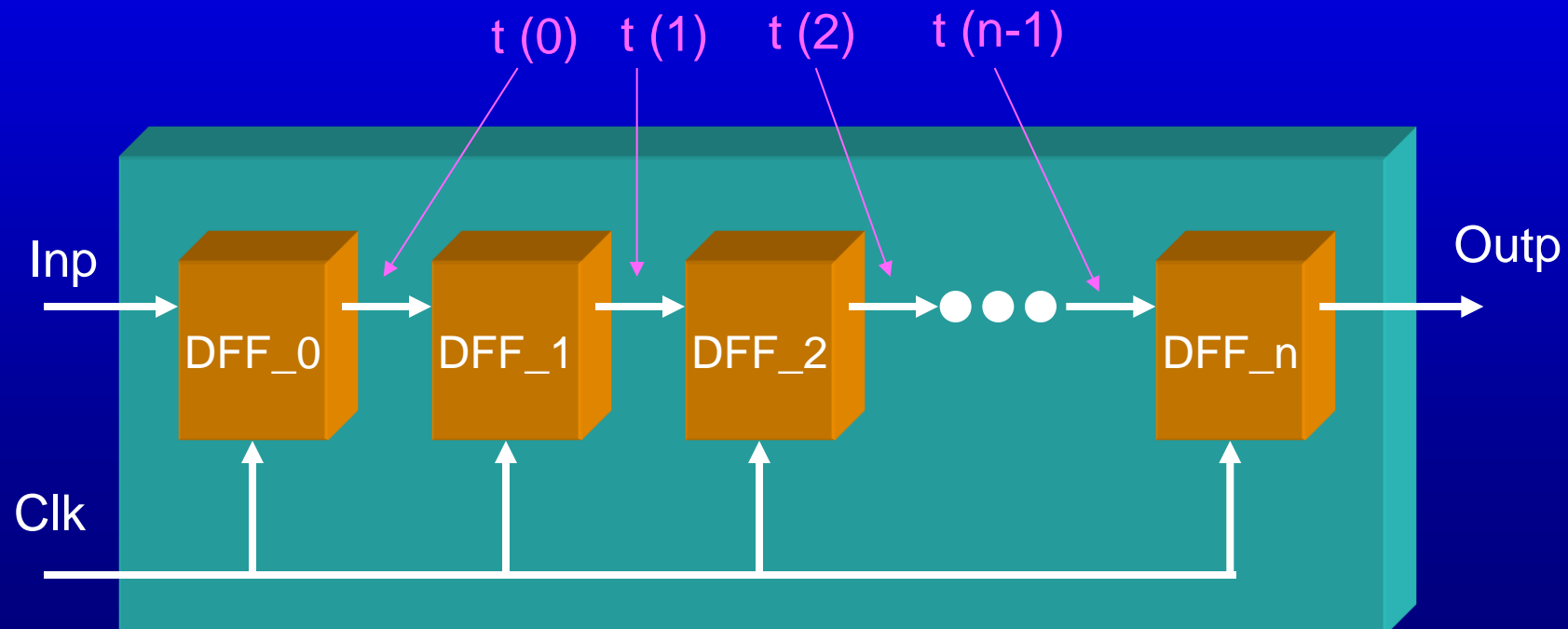Need intermediate  
signal  $t$  (0 to  $n-1$ )


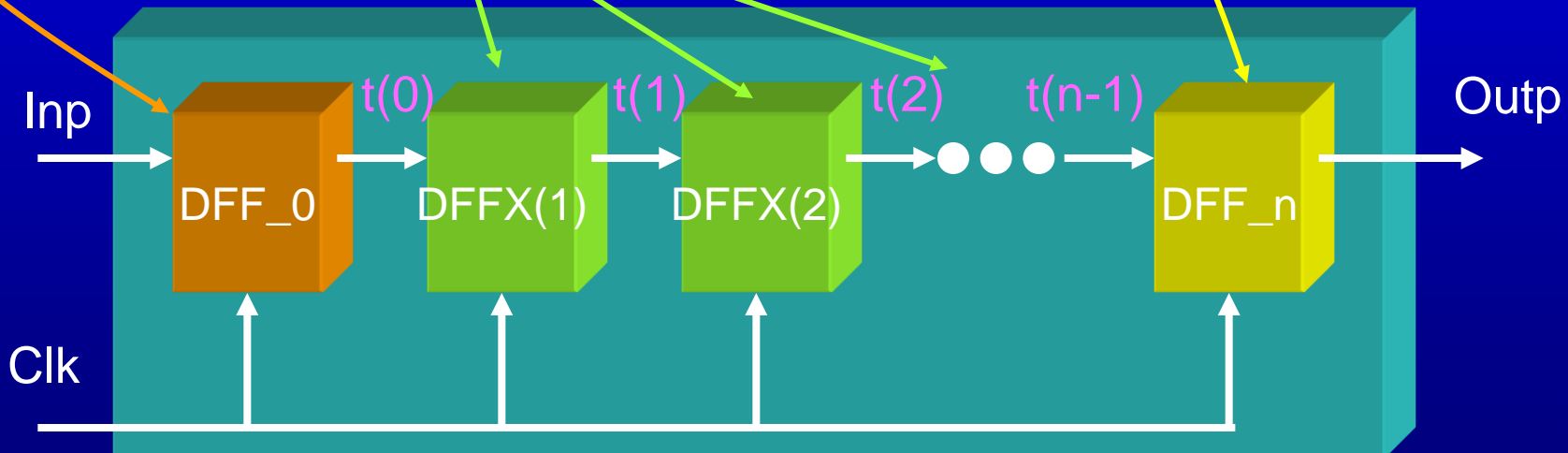
# GENERATE Statement

```
SIGNAL t: BIT_VECTOR (0 TO n-1);  
...  
dff_0: DFF PORT MAP (Inp, Clk, t (0));  
dff_n: DFF PORT MAP (t (n-1), Clk, Outp);  
FOR i IN 1 TO n-1 GENERATE  
  dffx: DFF PORT MAP ( t (i-1), Clk, t (i) );  
END GENERATE;
```



# Contents

- Introduction
- Signal assignment
- Modelling delays
- Describing behaviour
- Structure, test benches, libraries, parameterisation
- Standards

# VHDL Standards

- Std\_LOGIC 1164 Package
  - IEEE Standard
  - Supported by all VHDL simulation/synthesis tools
- VITAL
  - Modelling timing in VHDL



# 9-valued Logic Type: std\_ulogic

- **Modelling CMOS**
  - Current strengths
  - Tristating
- **Modelling Don't Care**
- **Simulation Values**
  - Unknown
  - Uninitialised

```
TYPE std_ulogic IS (  
    'U', -- uninitialised  
    'X', -- unknown  
    '0', -- Forcing 0  
    '1', -- Forcing 1  
    'Z', -- High impedance  
    'W', -- Weak Unknown  
    'L', -- Weak 0  
    'H', -- Weak 1  
    '-', -- Don't care  
);
```

# Signal Drivers

```
ARCHITECTURE x...  
SIGNAL a: BIT;  
begin  
  PROCESS  
  begin  
    ...  
    a <= '1';  
    ...a <= '0';...  
  end;  
  PROCESS  
  begin  
    ...  
    a <= '0';  
    ...  
  end;  
  a <= '0';  
end x;
```

Driver for a

Driver for a

Driver for a


Multiple drivers  
not allowed for  
same signal!  
- leads to conflicts

# Resolution Functions

- Multiple drivers allowed only when signal is declared to be **RESOLVED**
  - using RESOLUTION FUNCTION

```
FUNCTION res (values: BIT_VECTOR) RETURN BIT IS  
VARIABLE accum : BIT := '1';  
BEGIN  
  FOR i IN values'RANGE LOOP  
    accum := accum AND values(i);  
  END LOOP;  
  RETURN accum;  
END;
```

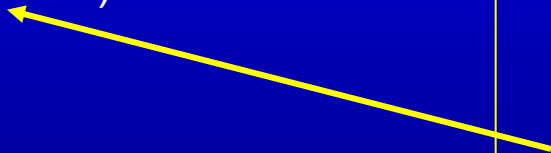Multiple driving  
values treated  
as vector



Modelling  
Wired AND



# Resolving std\_ulogic Signals

- Models the effect of shorting two wires in CMOS

```
TYPE stdlogic_table is array(std_ulogic, std_ulogic)
    of std_ulogic;
CONSTANT resolution_table : stdlogic_table := (
--  U    X    0    1    Z    W    L    H    -
('U', 'U', 'U', 'U', 'U', 'U', 'U', 'U', 'U' ), -- | U |
('U', 'X', 'X', 'X', 'X', 'X', 'X', 'X', 'X' ), -- | X |
('U', 'X', '0', 'X', '0', '0', '0', '0', '0' ), -- | 0 |
('U', 'X', 'X', '1', '1', '1', '1', '1', '1' ), -- | 1 |
('U', 'X', '0', '1', 'Z', 'W', 'L', 'H', 'Z' ), -- | Z |
('U', 'X', '0', '1', 'W', 'W', 'W', 'W', 'W' ), -- | W |
('U', 'X', '0', '1', 'L', 'W', 'L', 'W', 'L' ), -- | L |
('U', 'X', '0', '1', 'H', 'W', 'W', 'H', 'H' ), -- | H |
('U', 'X', '0', '1', 'Z', 'W', 'L', 'H', '-' )  -- | - | );
```

# Resolution Function for std\_ulogic

```
FUNCTION resolved ( s : std_ulogic_vector )  
  RETURN std_ulogic IS  
  VARIABLE result : std_ulogic := '-';-- weakest state default  
  BEGIN  
    IF (s'LENGTH = 1) THEN RETURN s(s'LOW);  
    ELSE -- Iterate through all inputs  
      FOR i IN s'RANGE LOOP  
        result := resolution_table(result, s(i));  
      END LOOP; -- Return the resultant value  
      RETURN result;  
    END IF;  
  END resolved;
```

# Resolved Type: std\_logic

- Multiple std\_ulogic types resolved into std\_logic type

```
SUBTYPE std_logic IS resolved std_ulogic;
```

```
...
```

```
SIGNAL x: std_logic;
```

```
...
```

```
x <= 'Z';
```

```
x <= '1';
```

```
-- No conflict. Value of x resolves to '1'
```

unresolved  
type

resolution  
function

resolved  
type

# Overloading

- Standard operators can be overloaded for std\_ulogic type

```
FUNCTION "and" (l, r: std_ulogic) RETURN UX01 IS  
BEGIN  
    RETURN (and_table (l, r)); -- 2-d constant array  
END "and";
```

# Utilities

- Type conversions
  - to\_Bit
  - to\_BitVector
  - to\_StdUlogic
  - to\_StdLogicVector
- Detecting Edges
  - rising\_edge
  - falling\_edge