

Started on Saturday, 21 August 2021, 10:05 AM

State Finished

Completed on Saturday, 21 August 2021, 10:10 AM

Time taken 4 mins 50 secs


Grade 10.00 out of 10.00 (100%)

Question 1

Correct

Mark 10.00 out of 10.00

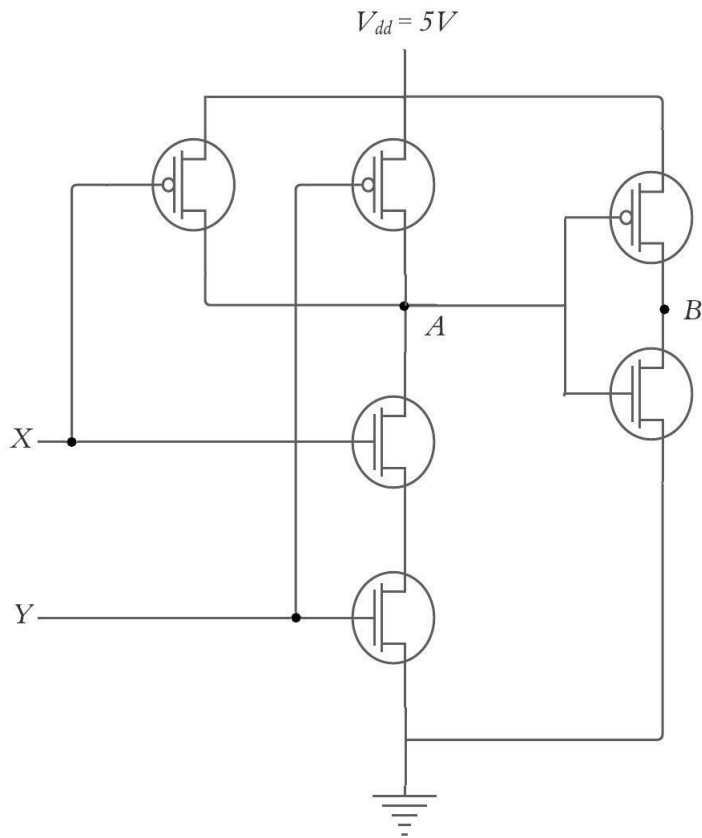In the following circuit, if the voltage values at X and Y are 0V and 5V, respectively, what will be the voltage values at A and B?



Select one:

- ☐ 0V and 0V
- ☐ 0V and 5V
- ☒ 5V and 0V ✓
- ☐ 5V and 5V

Your answer is correct.

The correct answer is: 5V and 0V