

Started on Tuesday, 12 October 2021, 10:05 AM

State Finished

Completed on Tuesday, 12 October 2021, 10:10 AM

Time taken 4 mins 54 secs

Marks 1.00/1.00


Grade 10.00 out of 10.00 (100%)

Question 1

Correct

Mark 1.00 out of 1.00

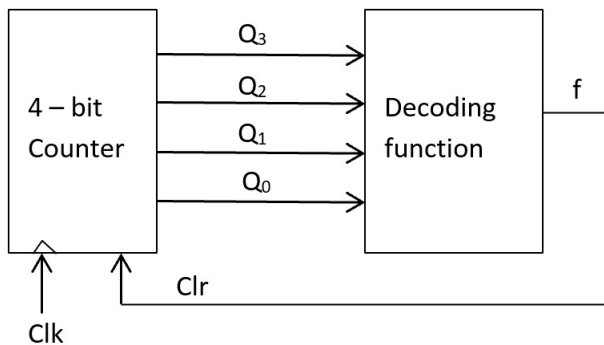A 4-bit modulo 16 counter can be used to implement a module 13 counter by using a suitable logic for clearing. See the block diagram given below. Note both counting up as well as clearing happens on the rising edge of the clock.



Which of the following presents the appropriate function that the decoder implements?

Select one:

- ☐ $f = Q_3 Q_2 Q_1 Q_0$
- ☒ $f = Q_3 Q_2 Q_1 Q_0'$ ✓
- ☐ None of the given options
- ☐ $f = Q_3 Q_2 Q_1' Q_0$
- ☐ $f = Q_3 Q_2 Q_1' Q_0'$

Your answer is correct.

The correct answer is: $f = Q_3 Q_2 Q_1' Q_0'$