

Started on	Tuesday, 7 September 2021, 10:05 AM
State	Finished
Completed on	Tuesday, 7 September 2021, 10:10 AM
Time taken	4 mins 59 secs
Marks	1.00/1.00
Grade	10.00 out of 10.00 (100%)

Question 1
Correct
Mark 1.00 out of 1.00

You need to use an 8:1 Multiplexer to implement the following function $f(a,b,c,d) = \sum m(0, 3, 5, 9, 10, 11, 12, 15)$. Considering that the inputs to the Multiplexer are numbered from 0 to 7, which of the following represents the correct sequence of values for the inputs numbered 1, 3, 5, and 7?

Select one:

- ☐ a', a, a, 0
- ☐ a, a, a', a
- ☐ 1, 1, a', a
- ☒ a, 1, a', a ✓

Your answer is correct.

The correct answer is: a, 1, a', a